




THE OHIO STATE UNIVERSITY

Impedance Tutorial

Wu Group
Billy McCulloch



UV-Vis Spectroscopy

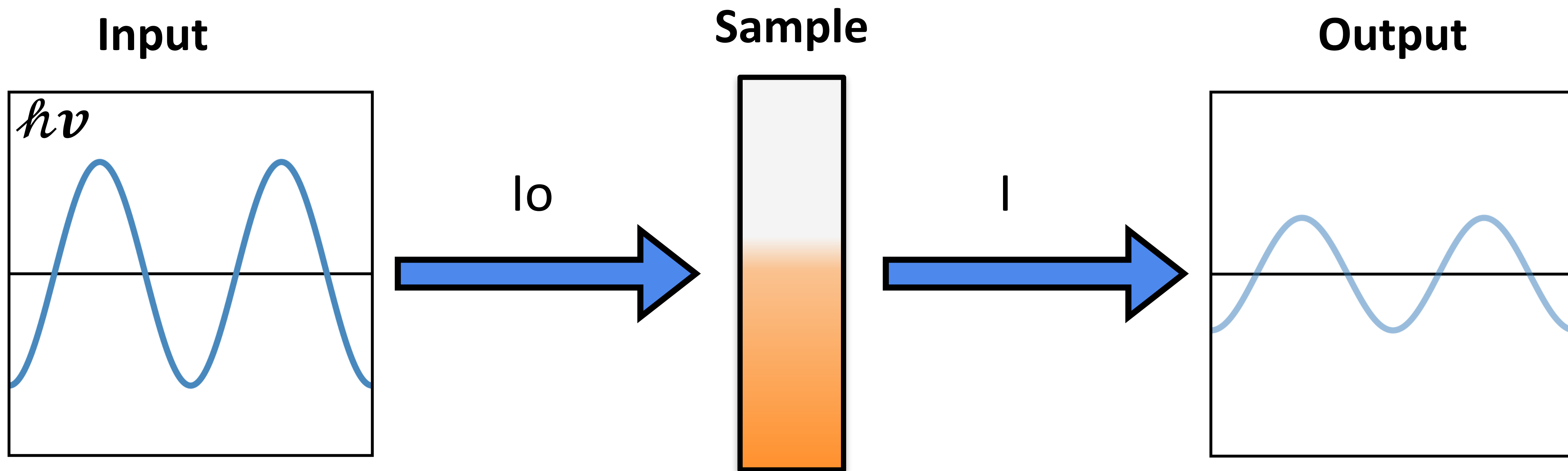




- Scan Frequency: $\sim 3-8 \times 10^{14}$ Hz
- Change in Amplitude of signal- Related to the Transmittance(ν)
- Gain Information about the effect of frequency on the sample



Input Voltage Signal

Sample Cell


Output Current Signal

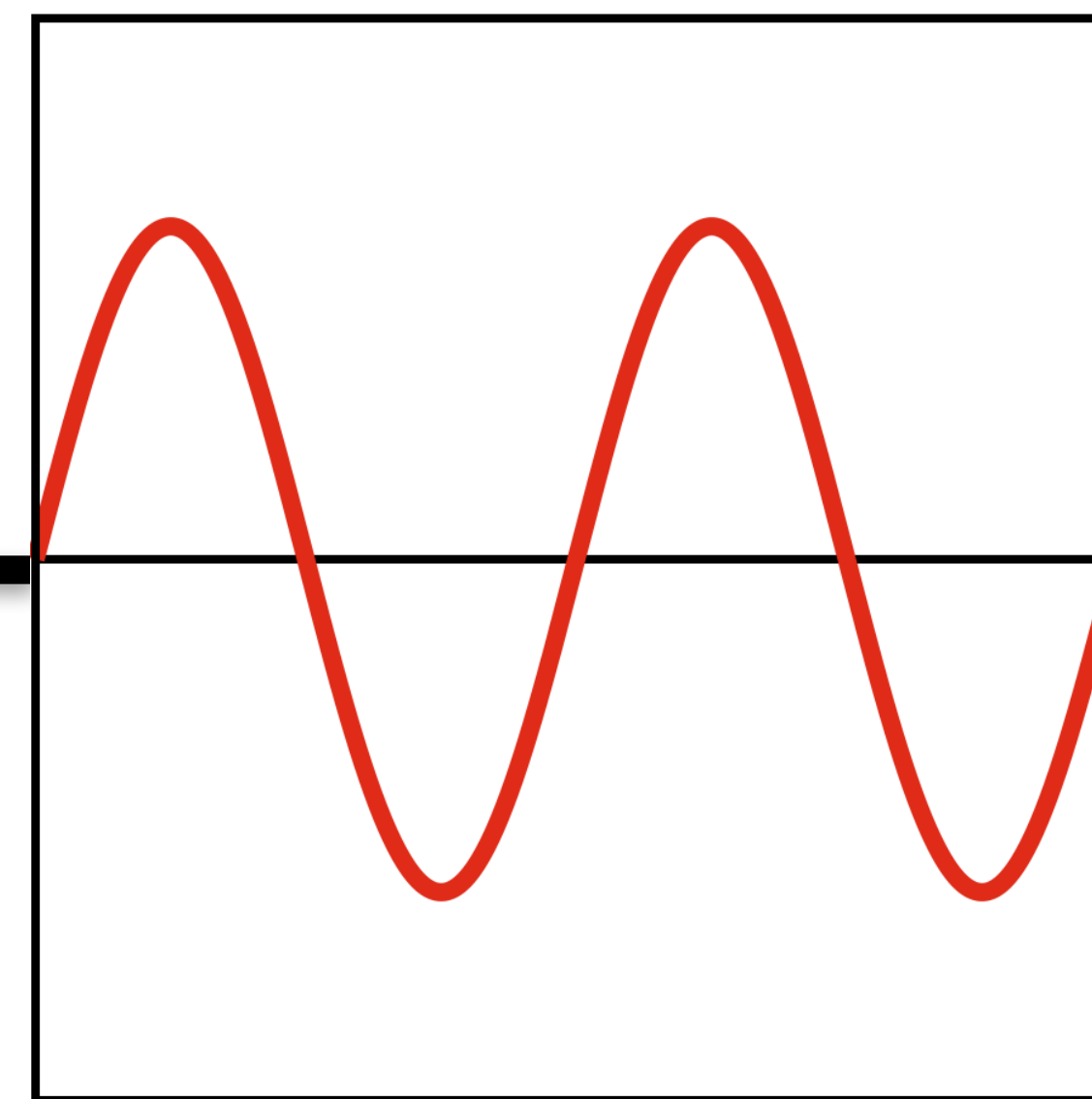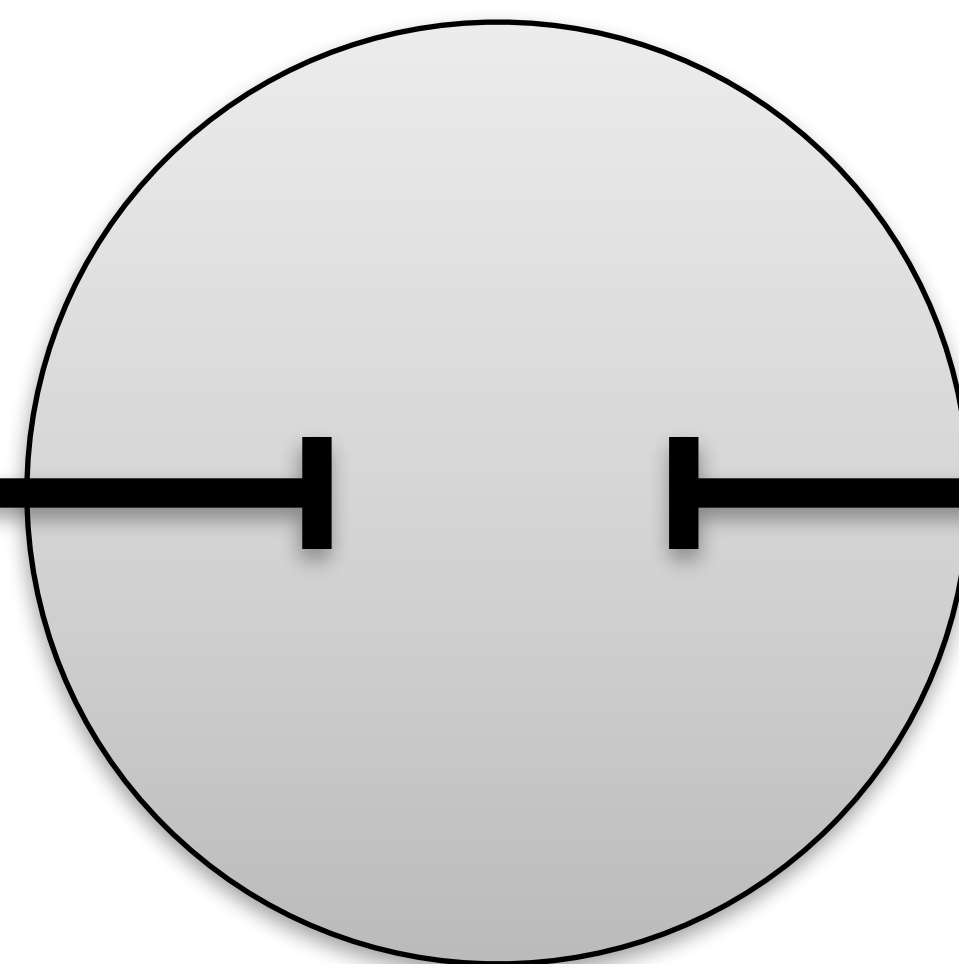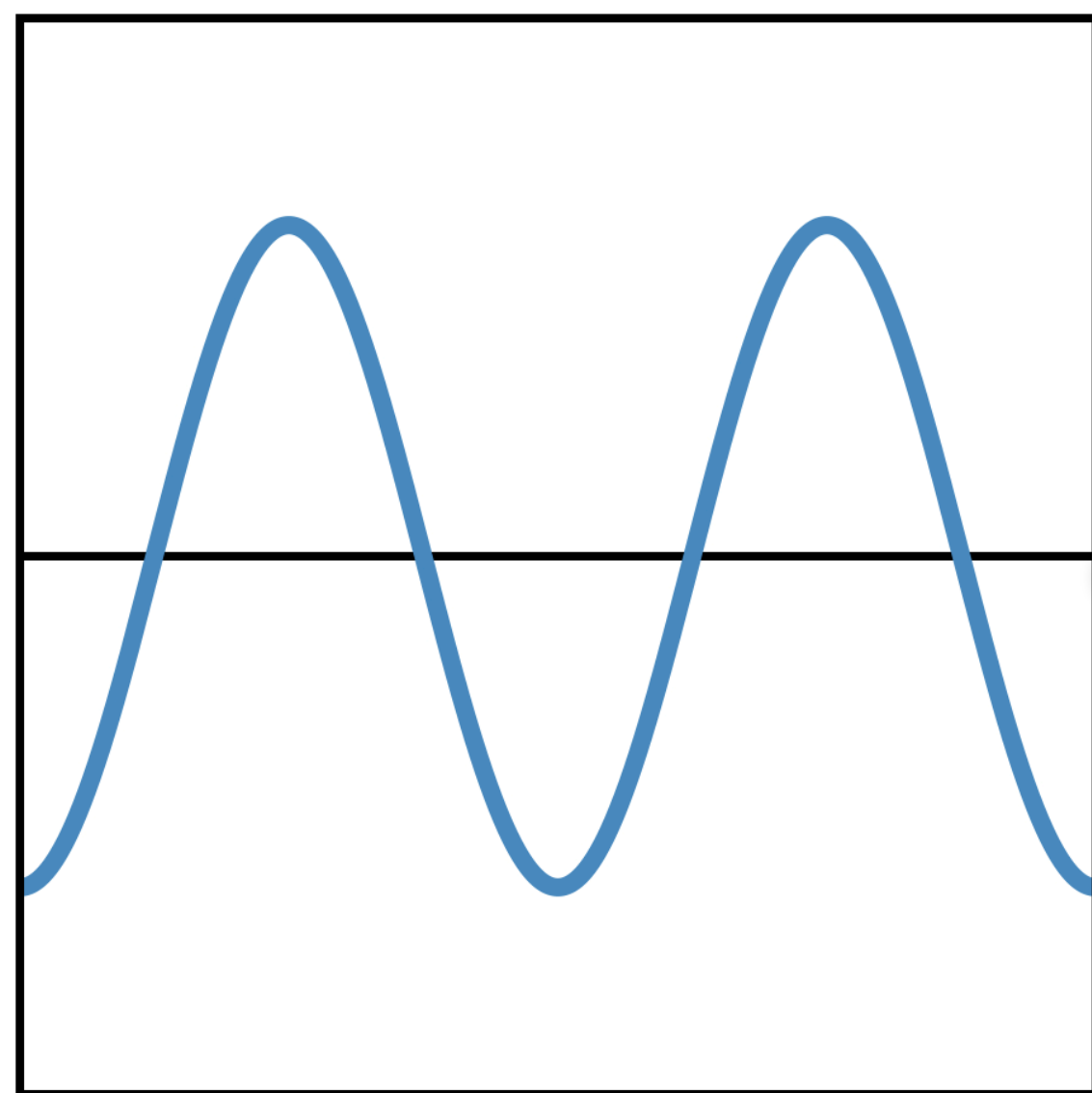

- Scan Frequency: $\sim 0.01 - 1$ MHz
- Change in Amplitude and phase related to the Impedance(ν)
- Different elements respond differently to different Frequencies



Dependence of Resistor

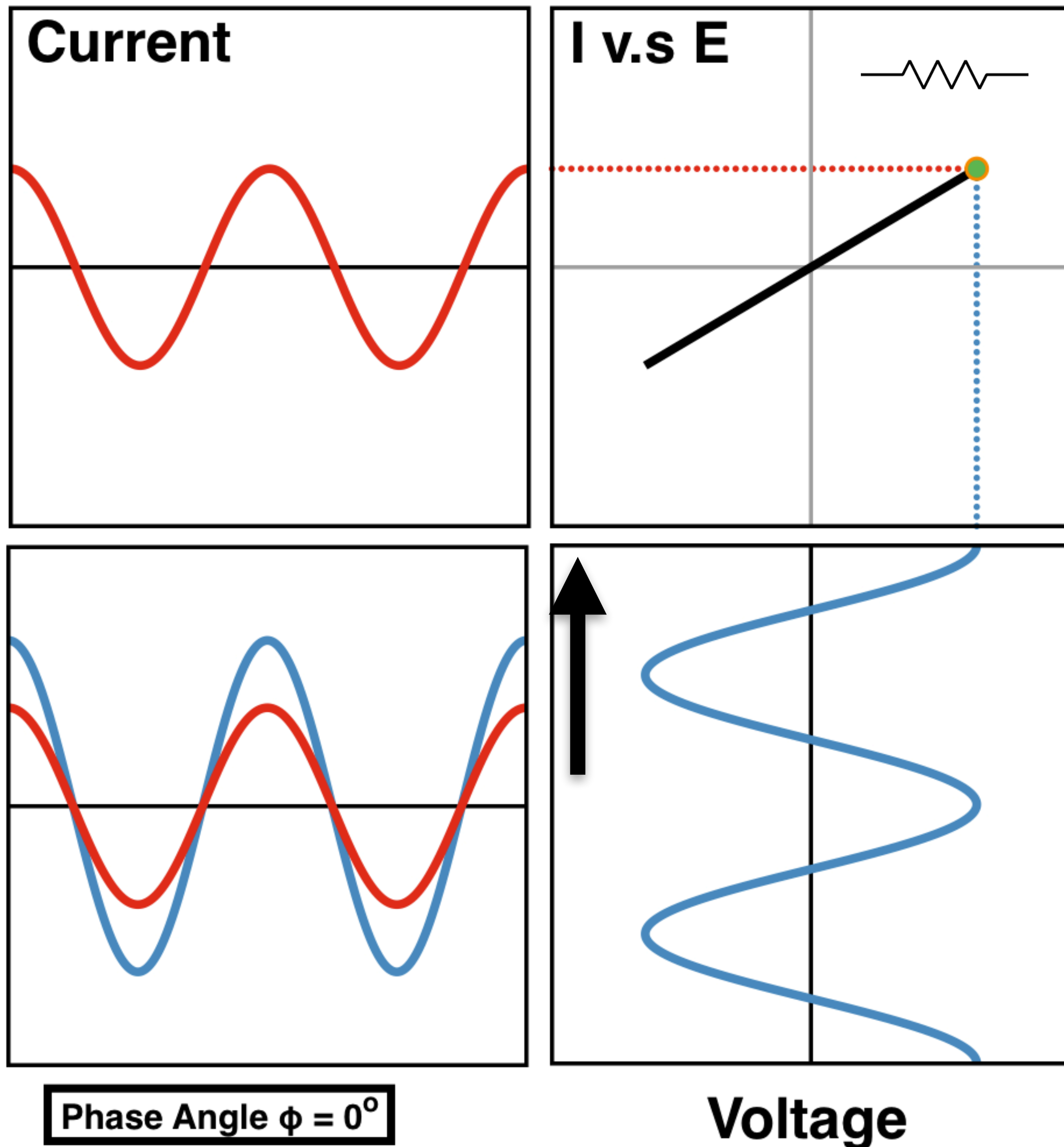

Resistor



Ohms Law $R = \frac{V}{I}$ $Z = \frac{V(t)}{I(t)}$





$V(t) = \sin(\omega t)$ **Input Voltage**

$I(t) = \frac{\sin(\omega t)}{R}$ **Output Current**

$Z_{resistor} = R$
 $Phase \phi = 0^\circ$



Dependence of a Capacitor

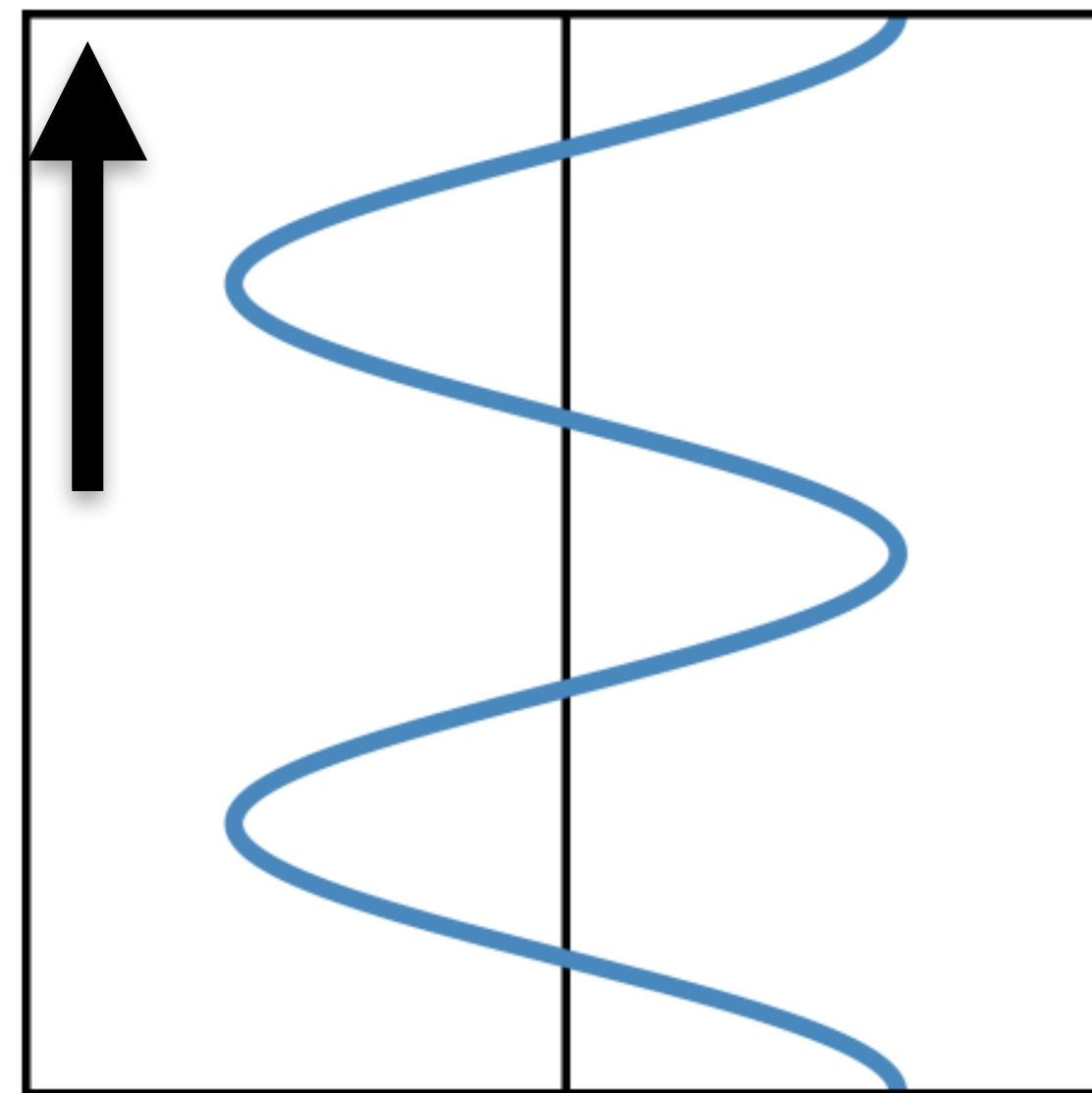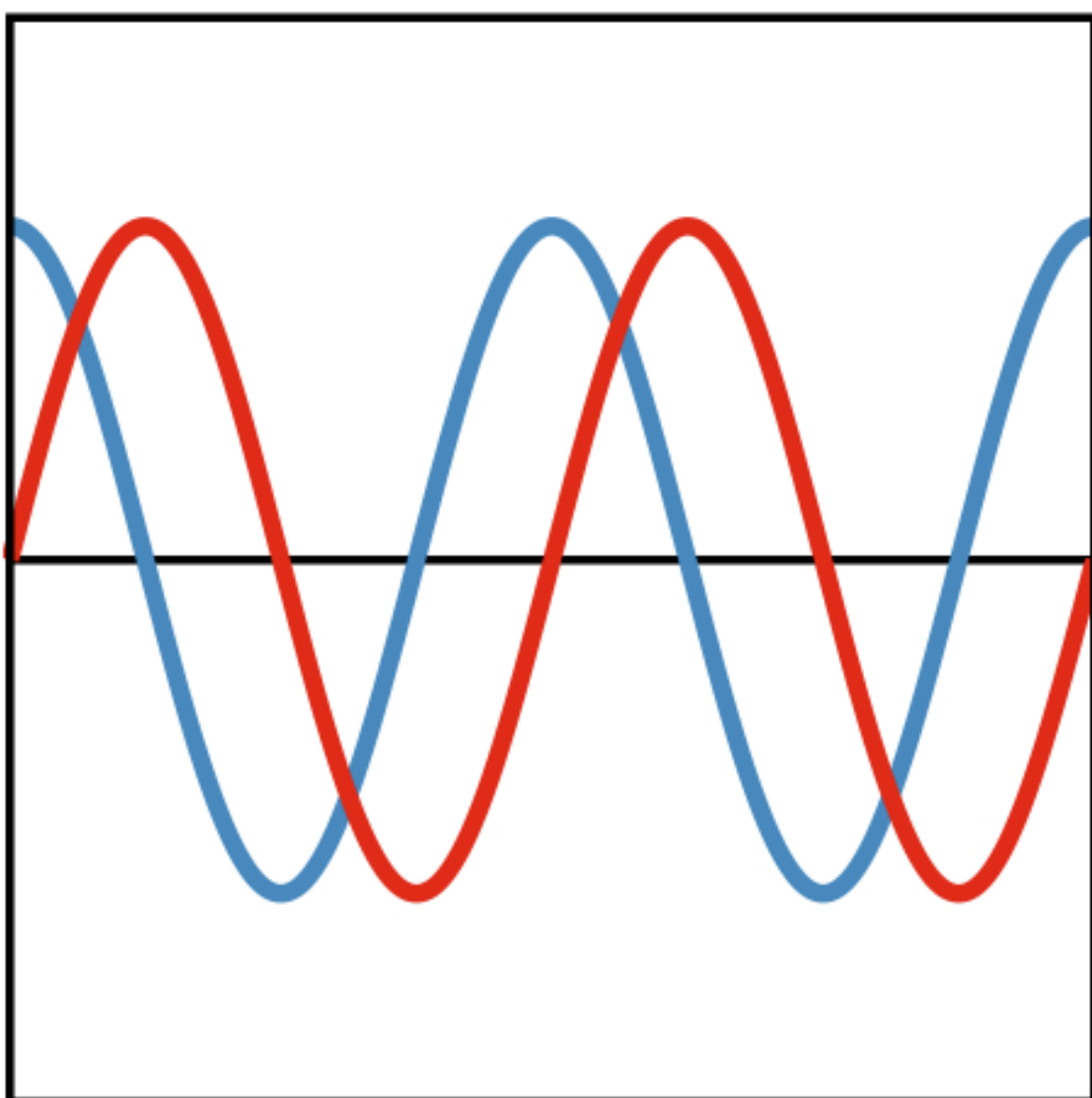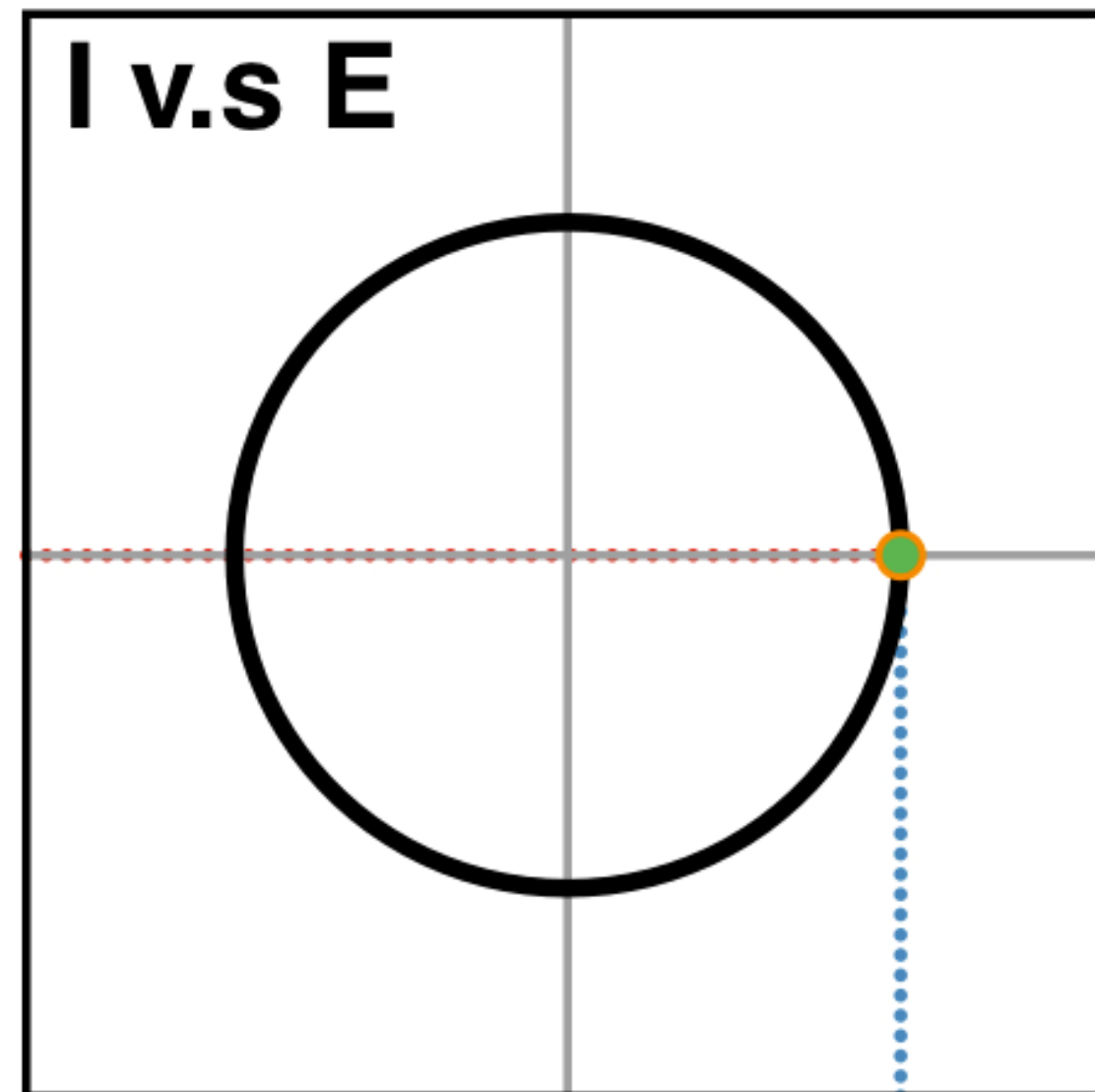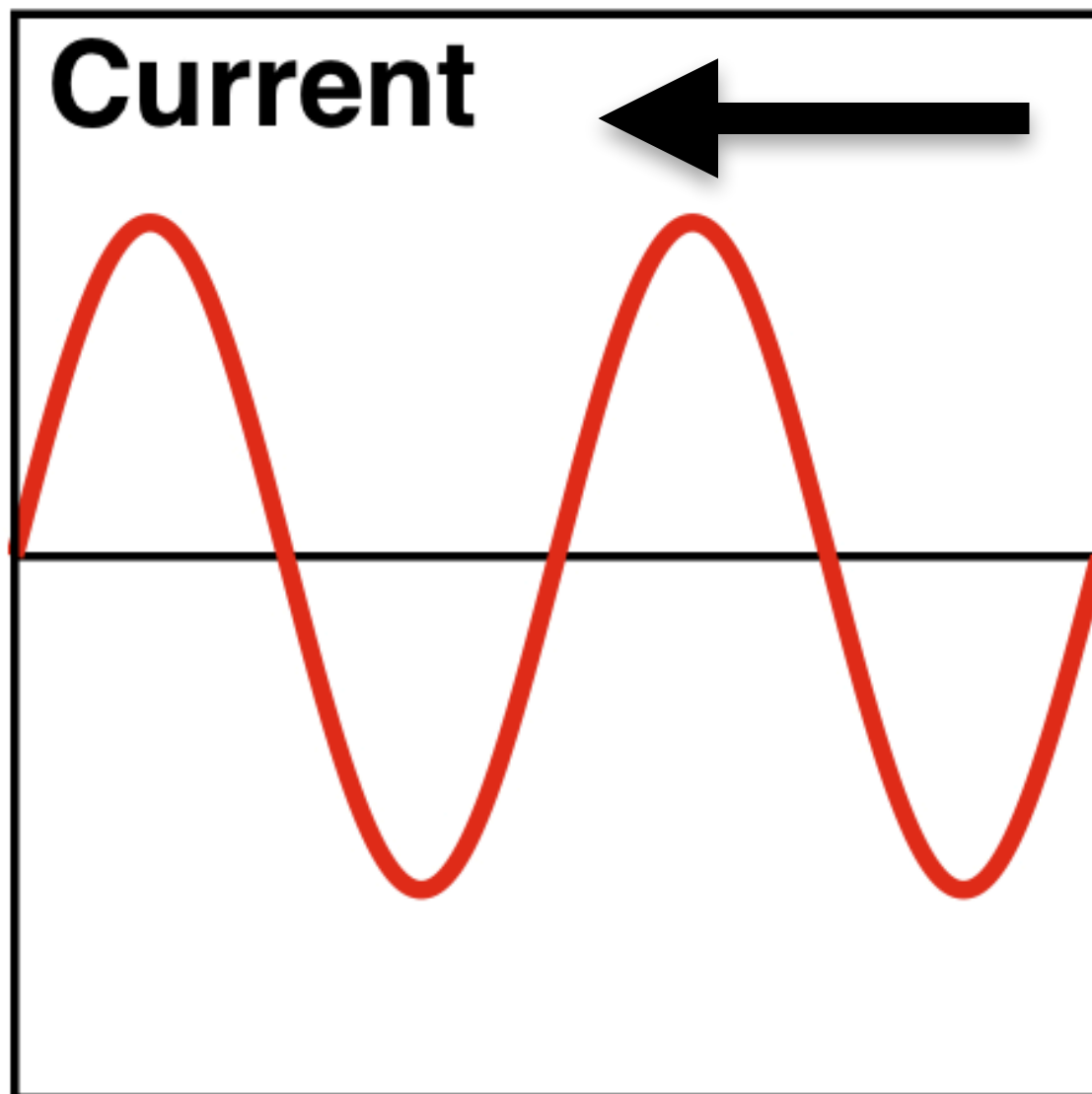

Phase Angle $\phi = -90^\circ$

Voltage

Capacitor

$$Q = CV$$

$$\frac{dQ}{dt} = C \frac{dV}{dt}$$

$$I(t) = C \frac{dV}{dt}$$

$$I(t) = C\omega \sin(\omega t + 90^\circ)$$

$$Z = \frac{V(t)}{I(t)}$$



$$V(t) = \sin(\omega t)$$



$$I(t) = C\omega \cos(\omega t)$$

$$Z_{\text{Capacitor}} = \frac{1}{\omega C}$$

$$\text{Phase } \phi = 90^\circ$$





How to Visualize the Data?

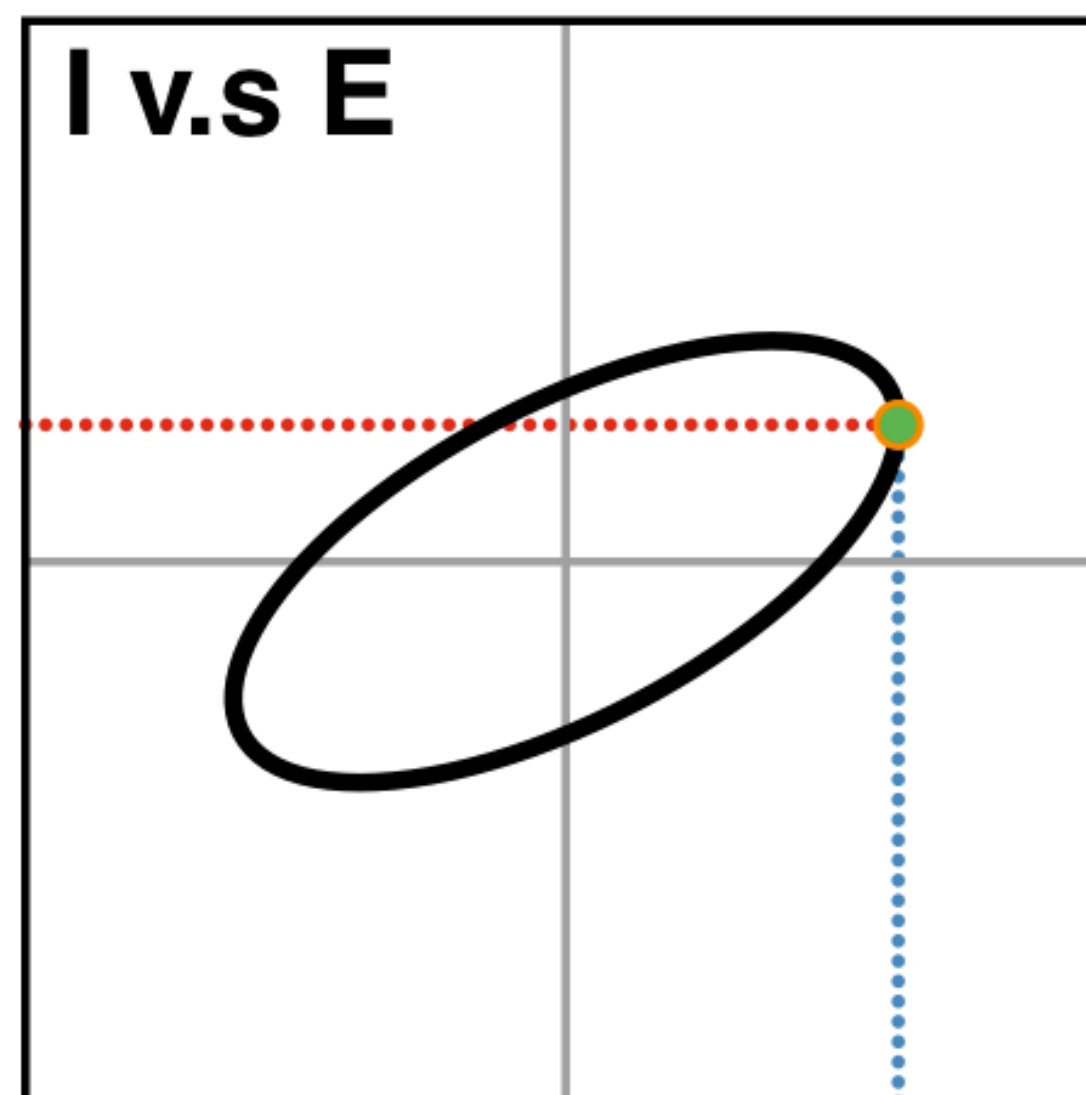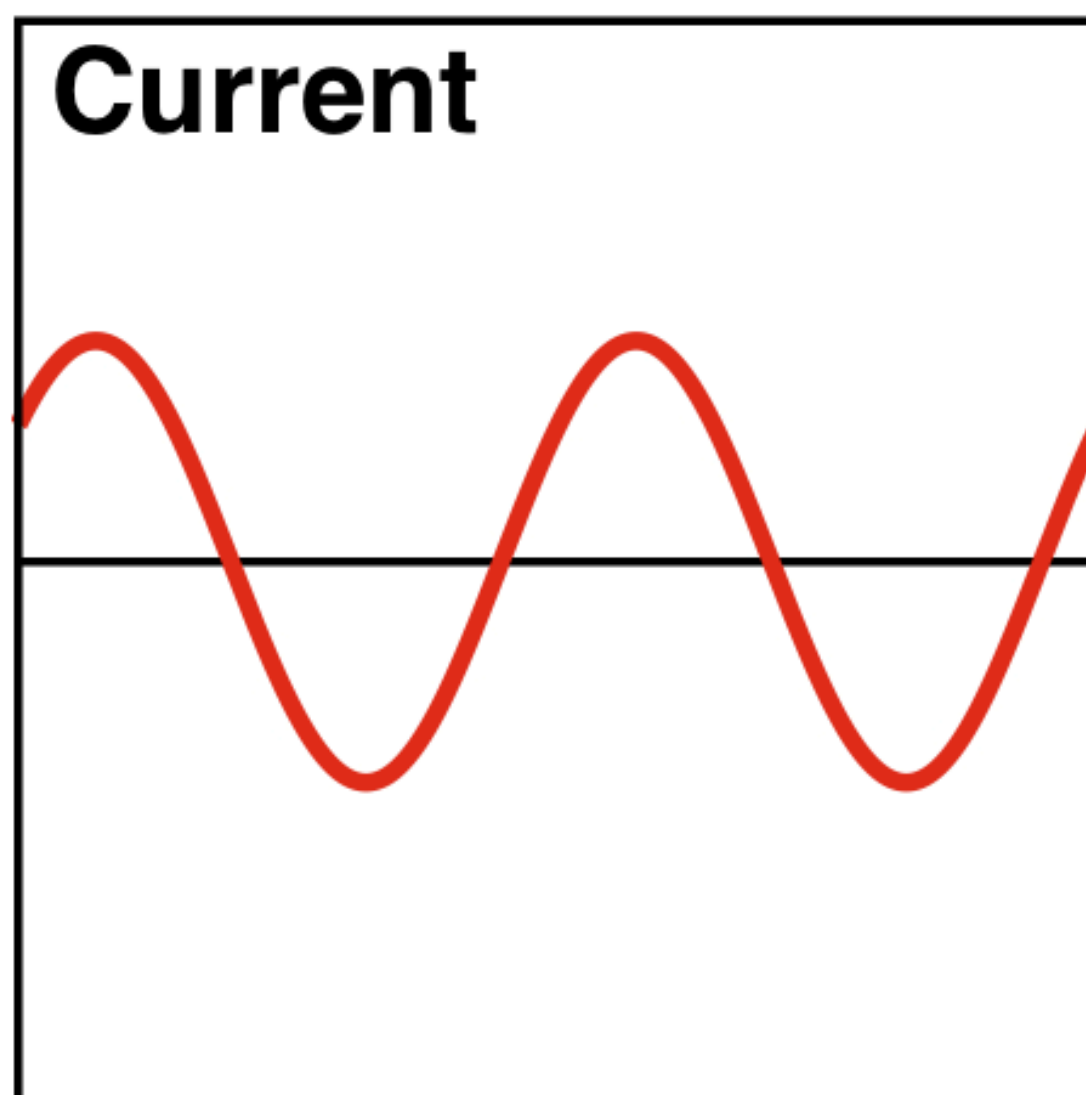


$$Z = \frac{E_t}{I_t} = \frac{E_o \sin(\omega t)}{I_o \sin(\omega t + \phi)} = Z_o \frac{\sin(\omega t)}{\sin(\omega t + \phi)}$$

Magnitude, Z_o Phase Angle, ϕ

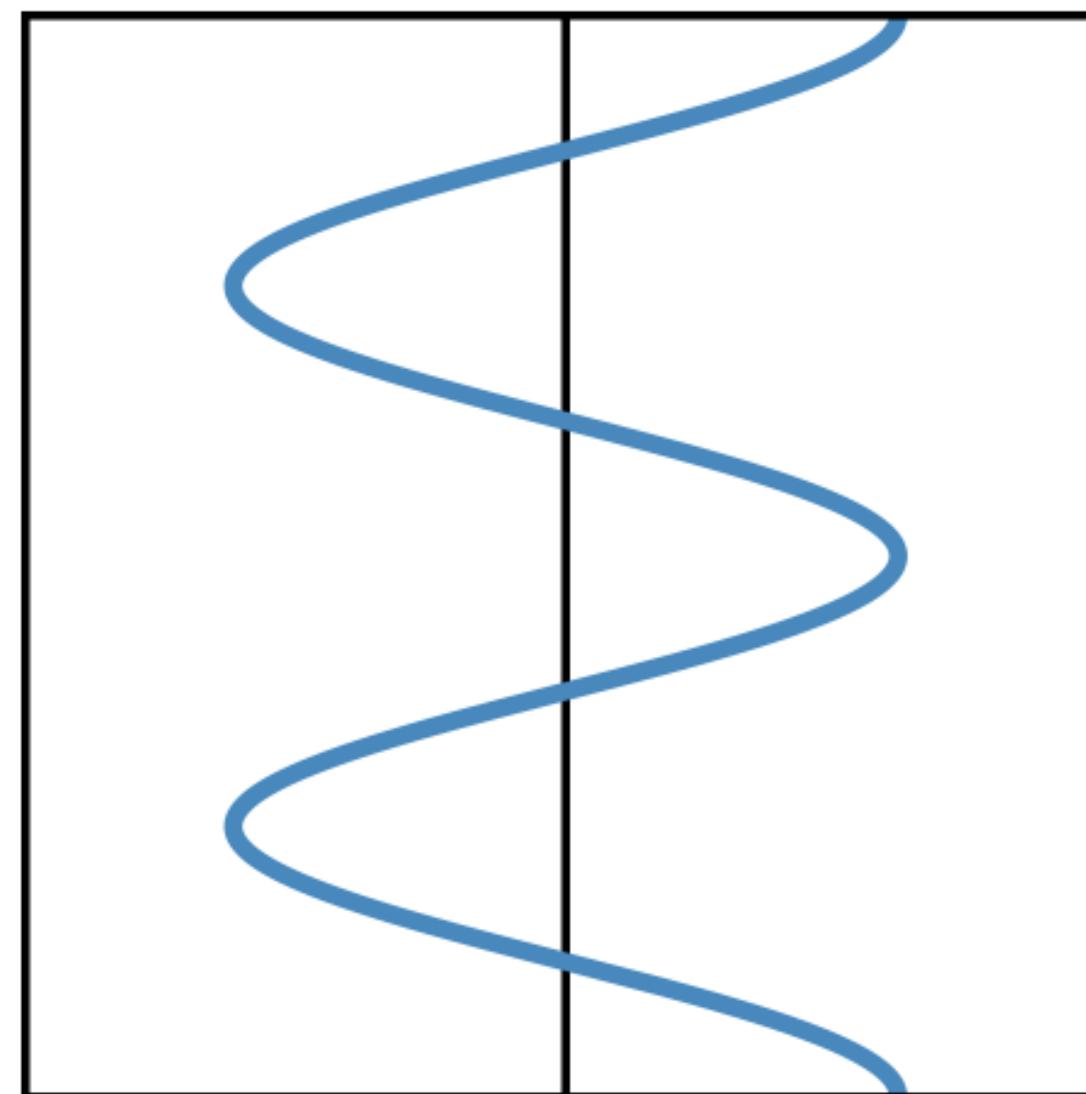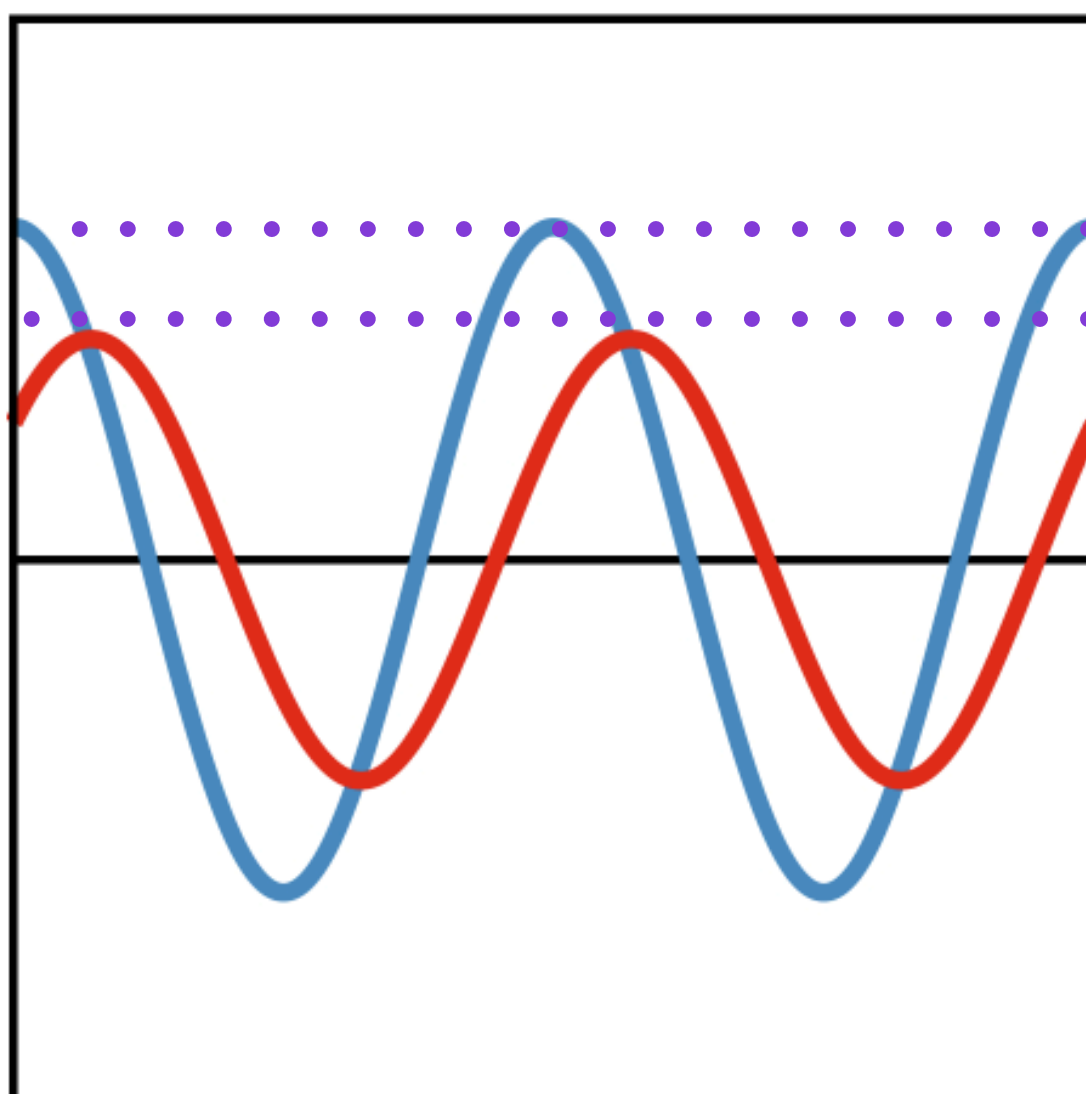


Phase Angle $\phi = -51.7^\circ$

Voltage

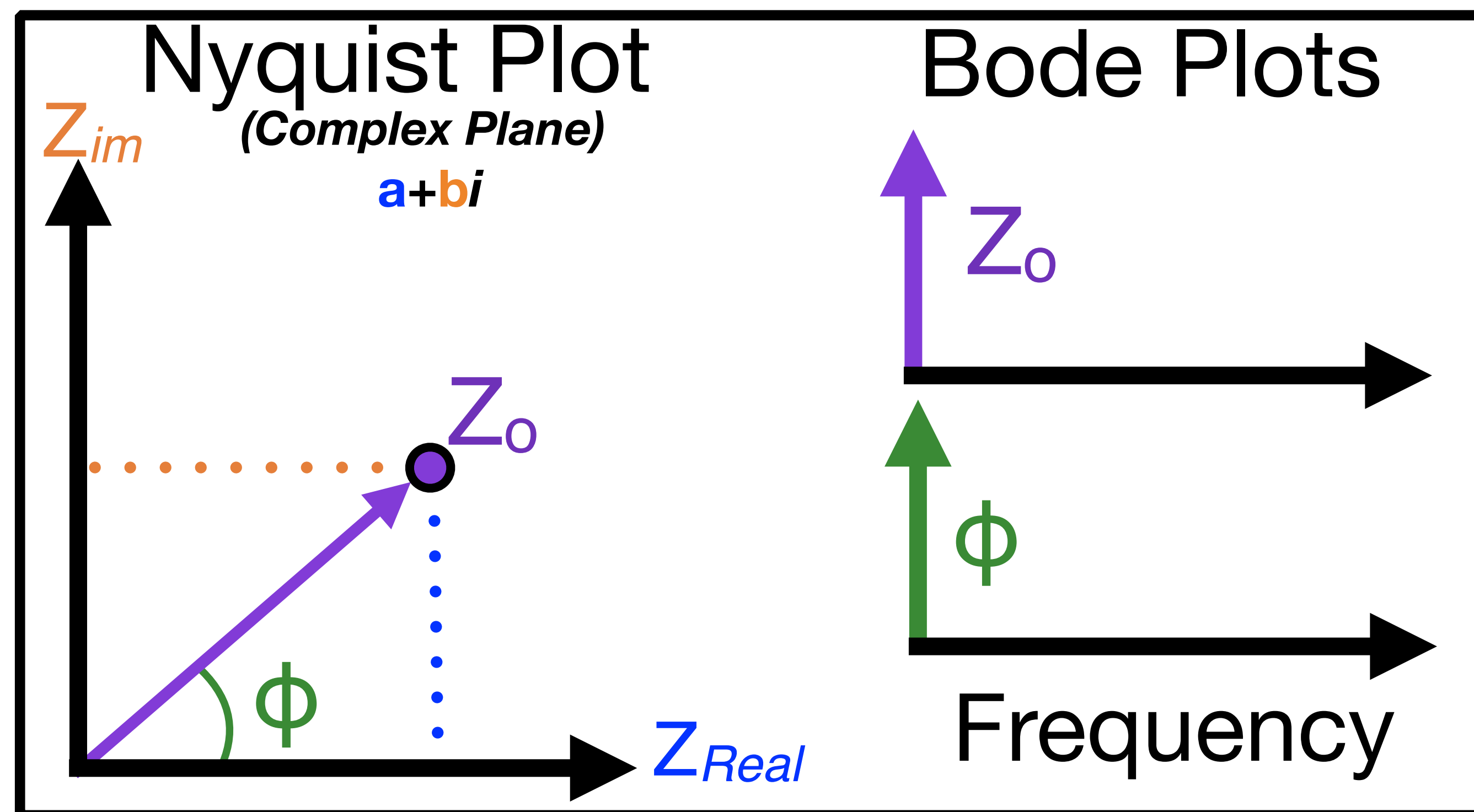





Common Electrode-Electrolyte System

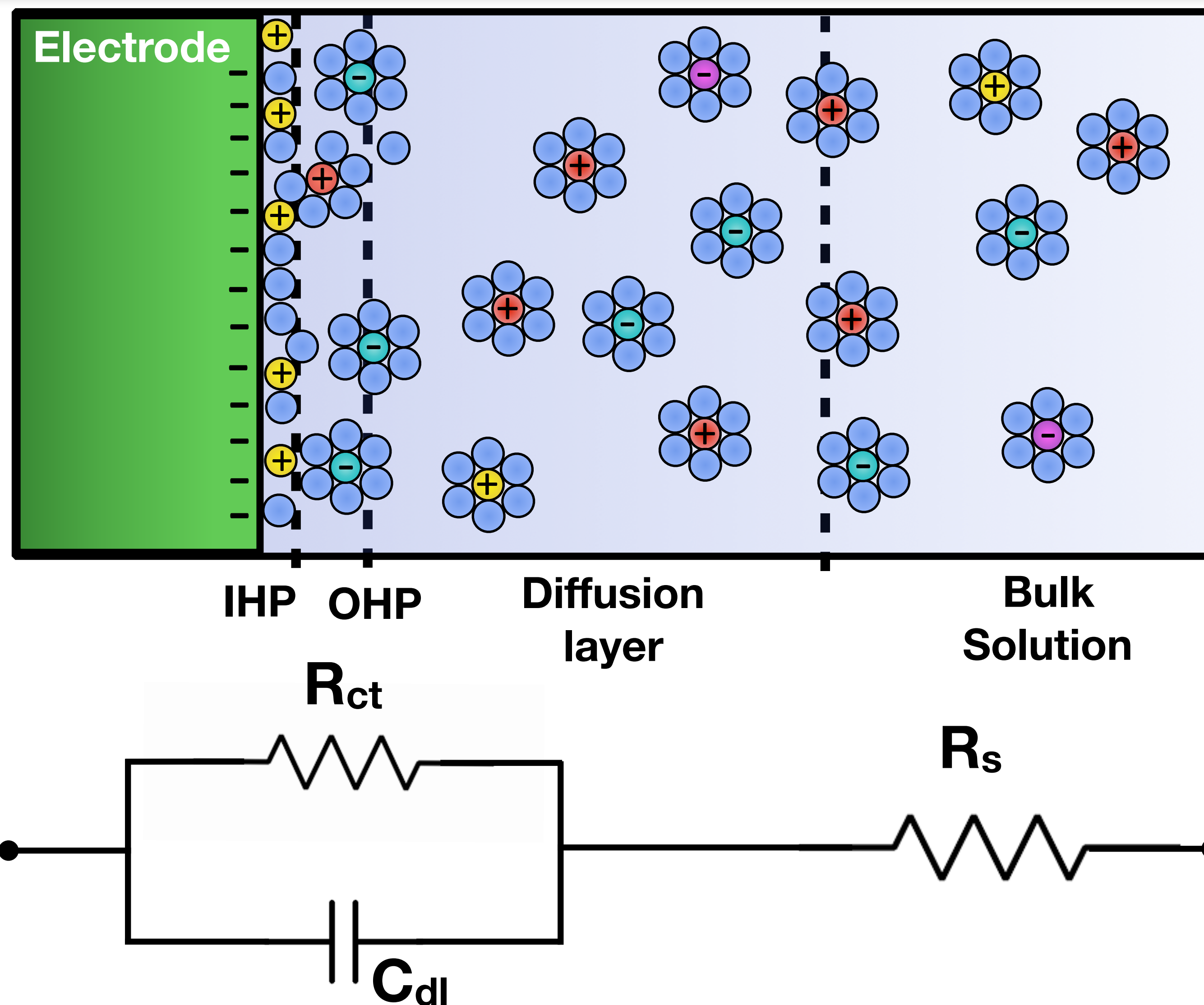

- **Faradaic Current**

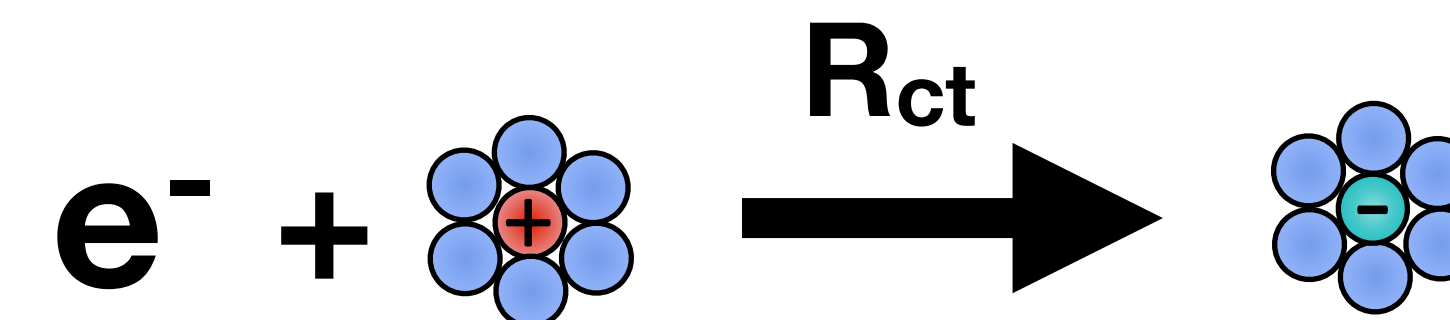


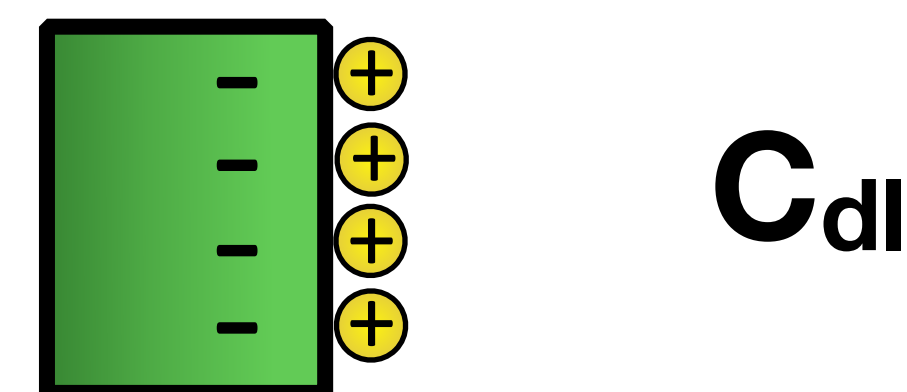- **Nonfaradaic Current**
(*Capacitive Charging*)






Frequency Dependent Circuit

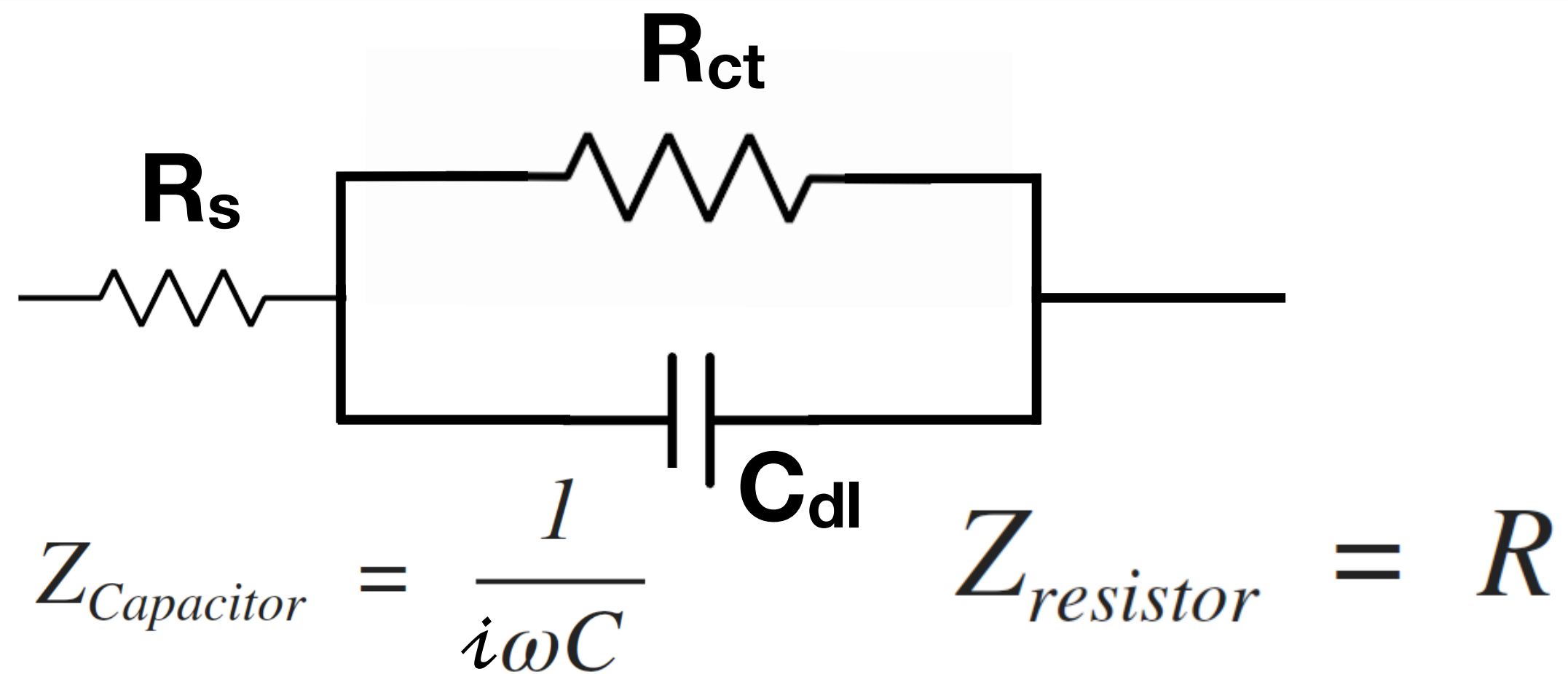


High Frequency $\omega \rightarrow \infty$
 $Z_{\text{Capacitor}} \rightarrow 0$

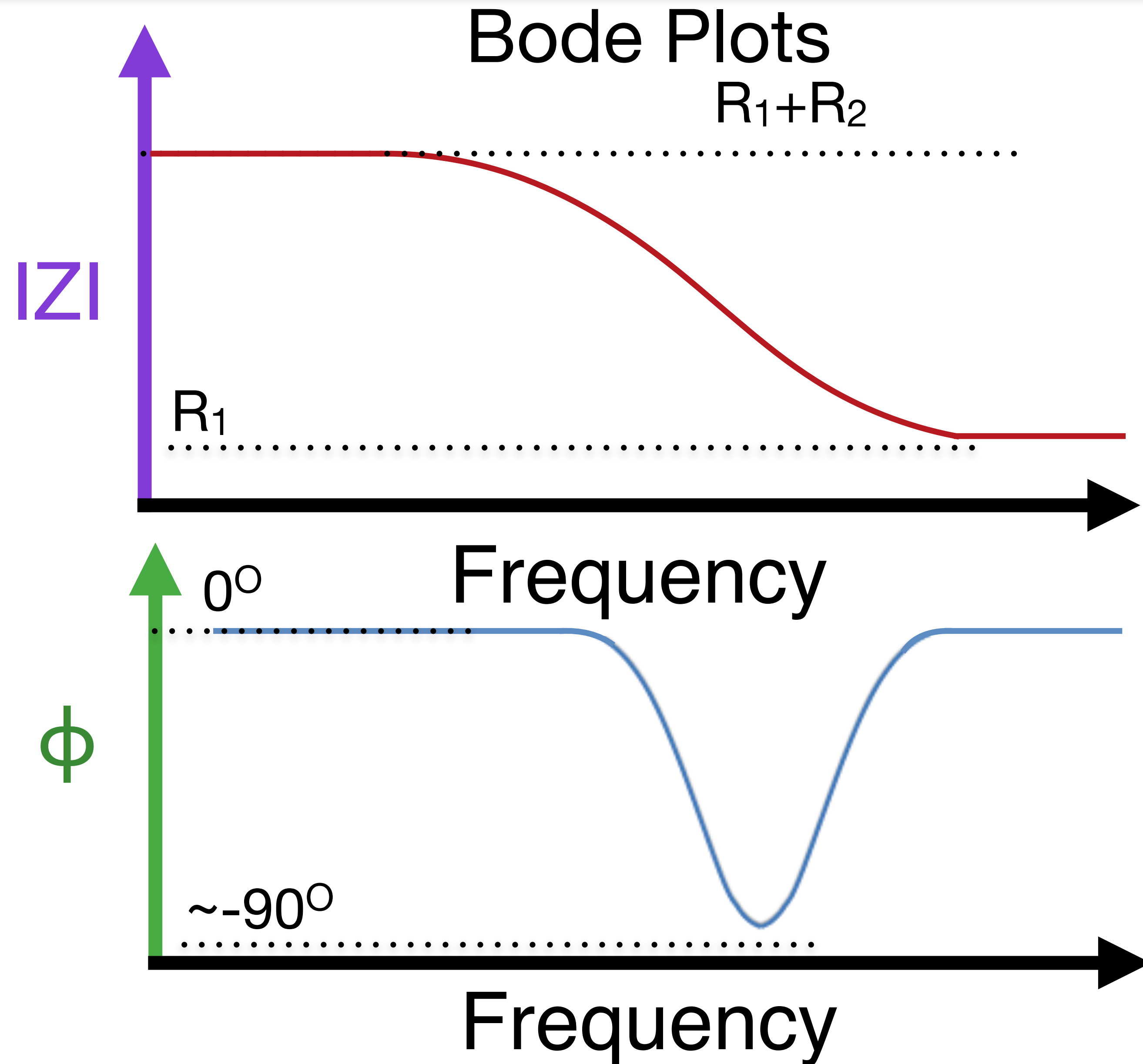
Low Frequency $\omega \rightarrow 0$
 $Z_{\text{Capacitor}} \rightarrow \infty$



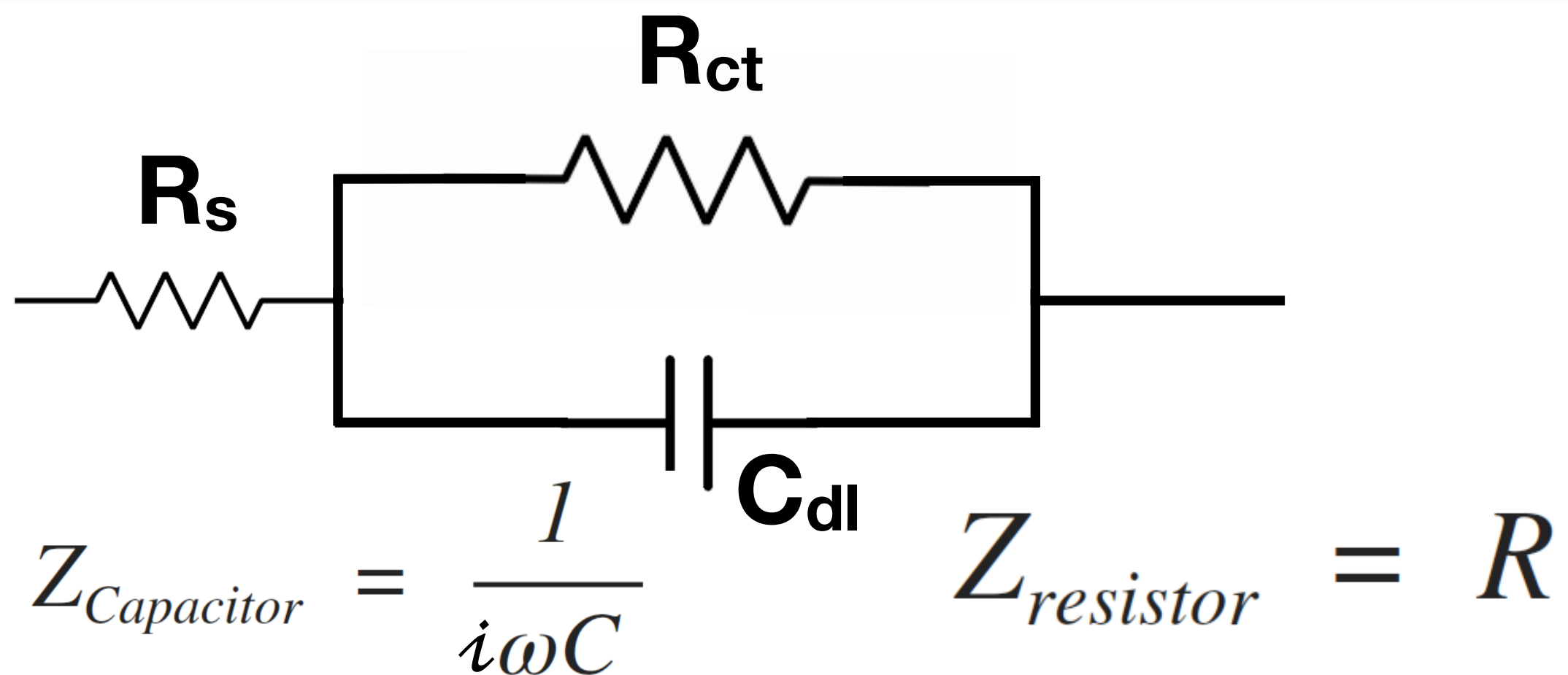
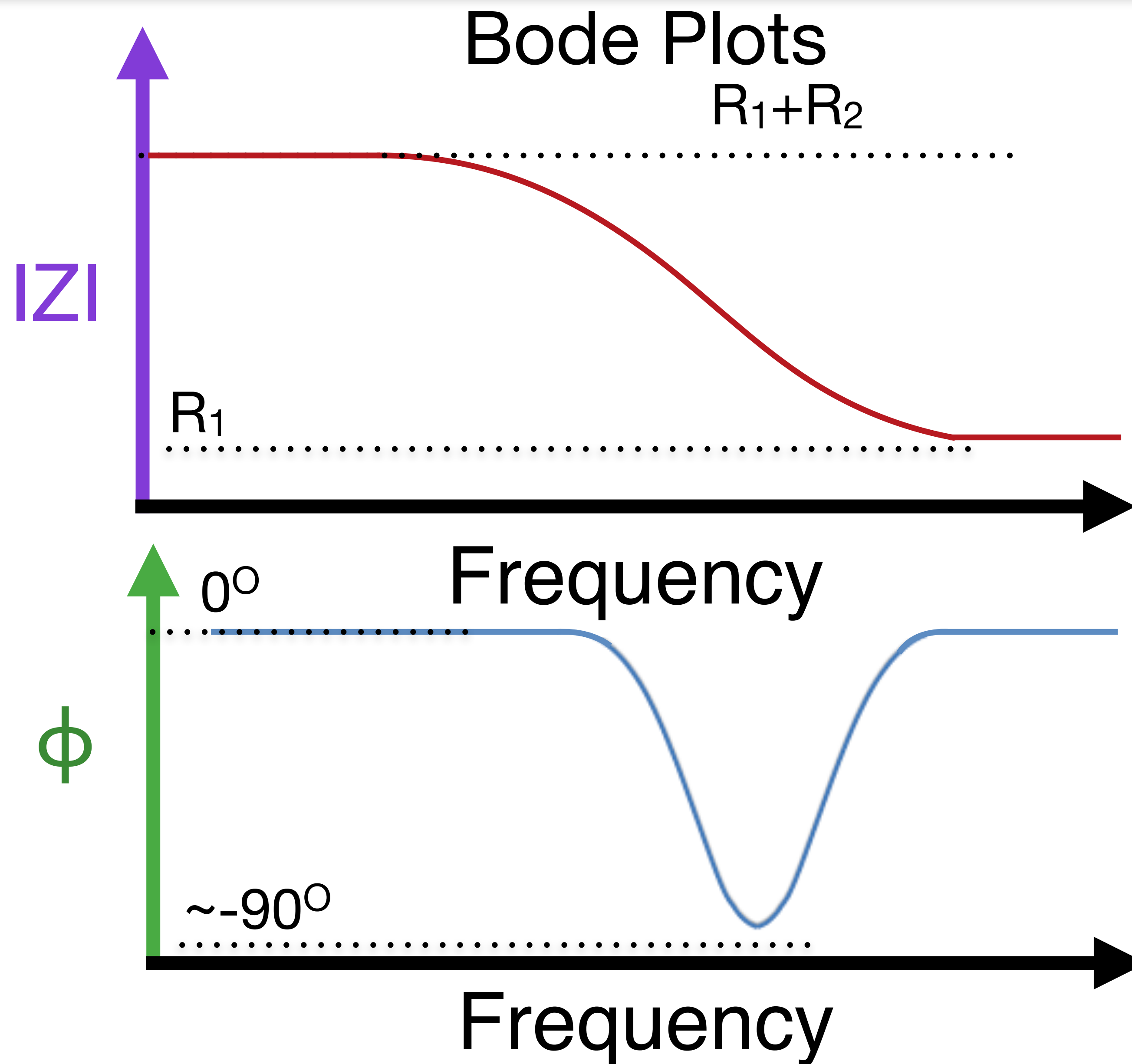


Frequency Dependent Circuit



High Frequency $\omega \rightarrow \infty$
 R_s
“Looks like” 


Low Frequency $\omega \rightarrow 0$
 R_s R_{ct}
“Looks like” 






Frequency Dependent Circuit

Nyquist Plot

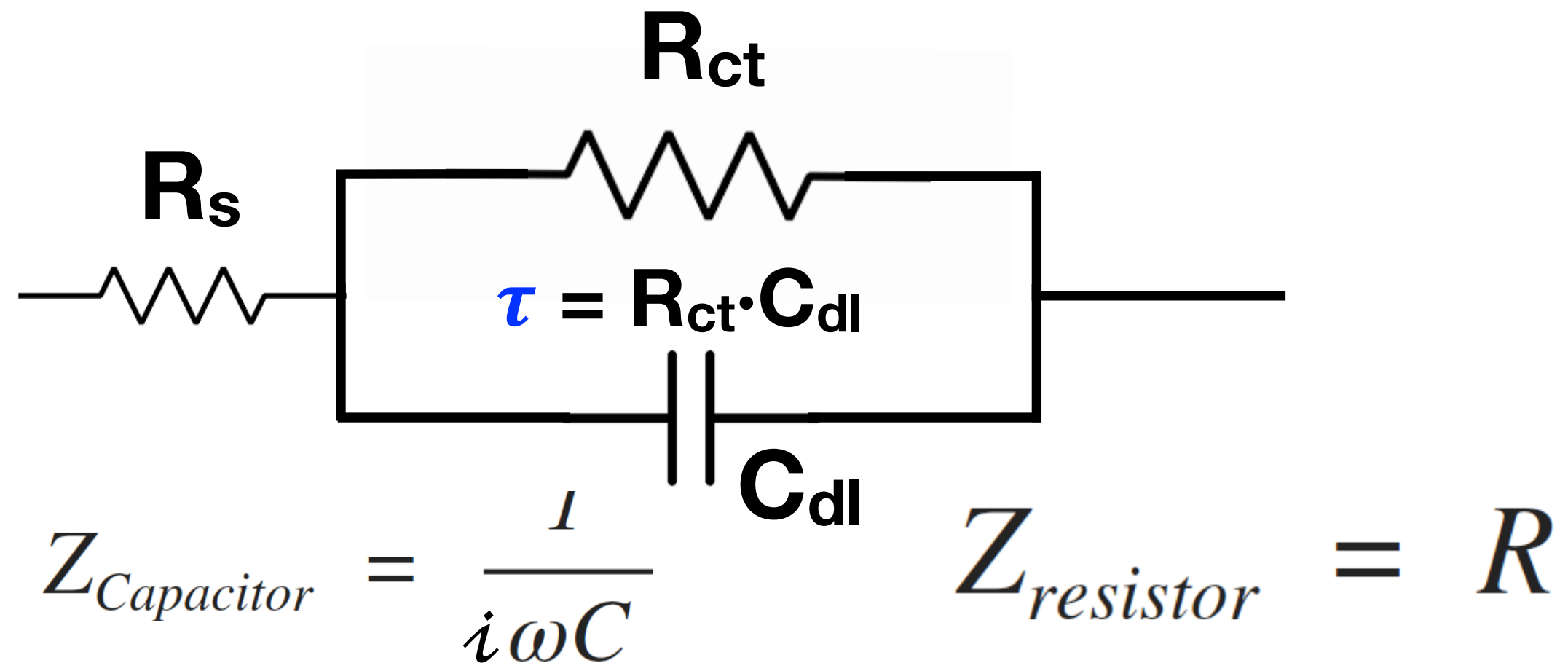

High Frequency $\omega \rightarrow \infty$
 $Z_{Capacitor} \rightarrow 0$

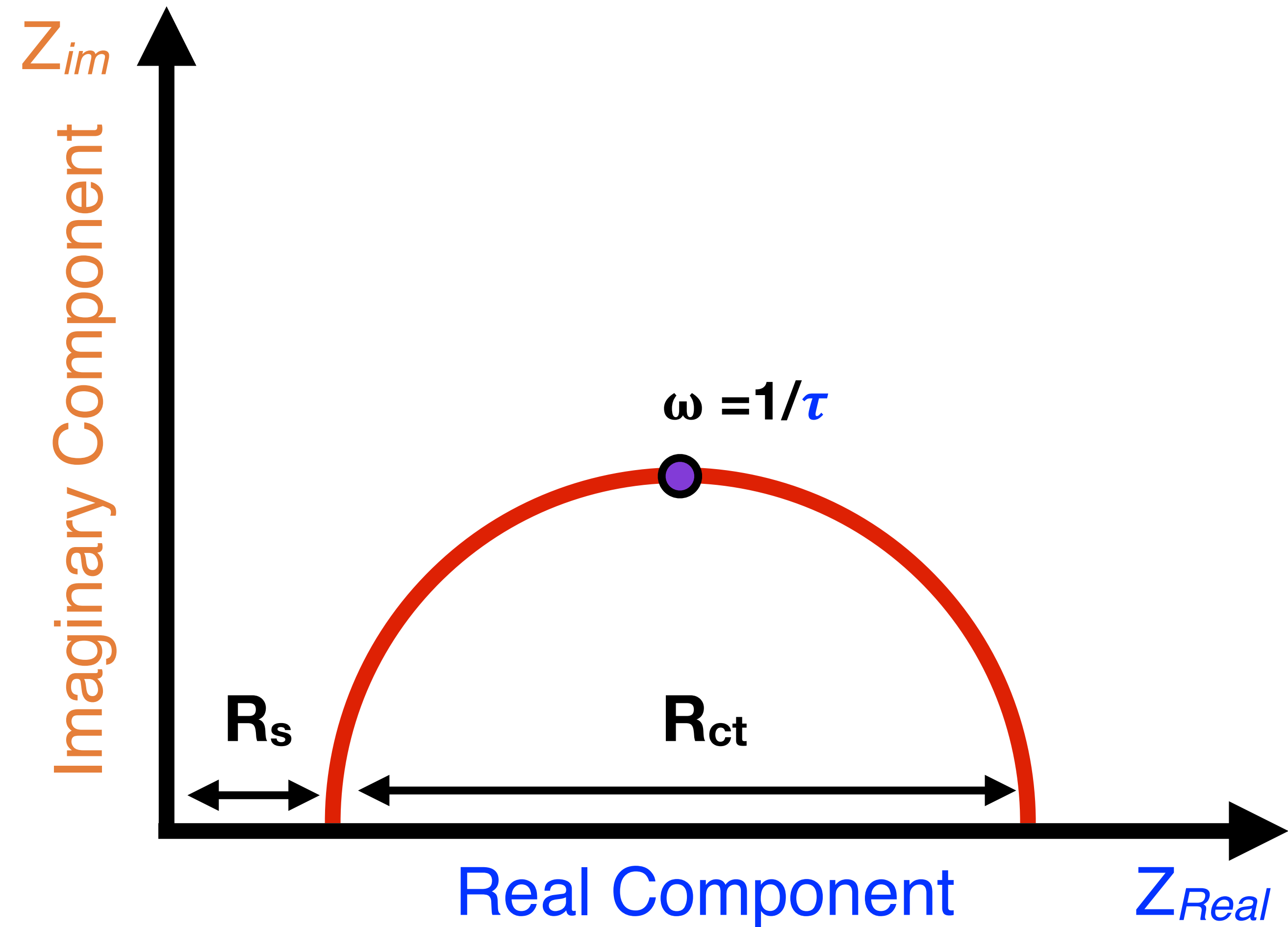Low Frequency $\omega \rightarrow 0$
 $Z_{Capacitor} \rightarrow \infty$







Running The Experiment


DEMO

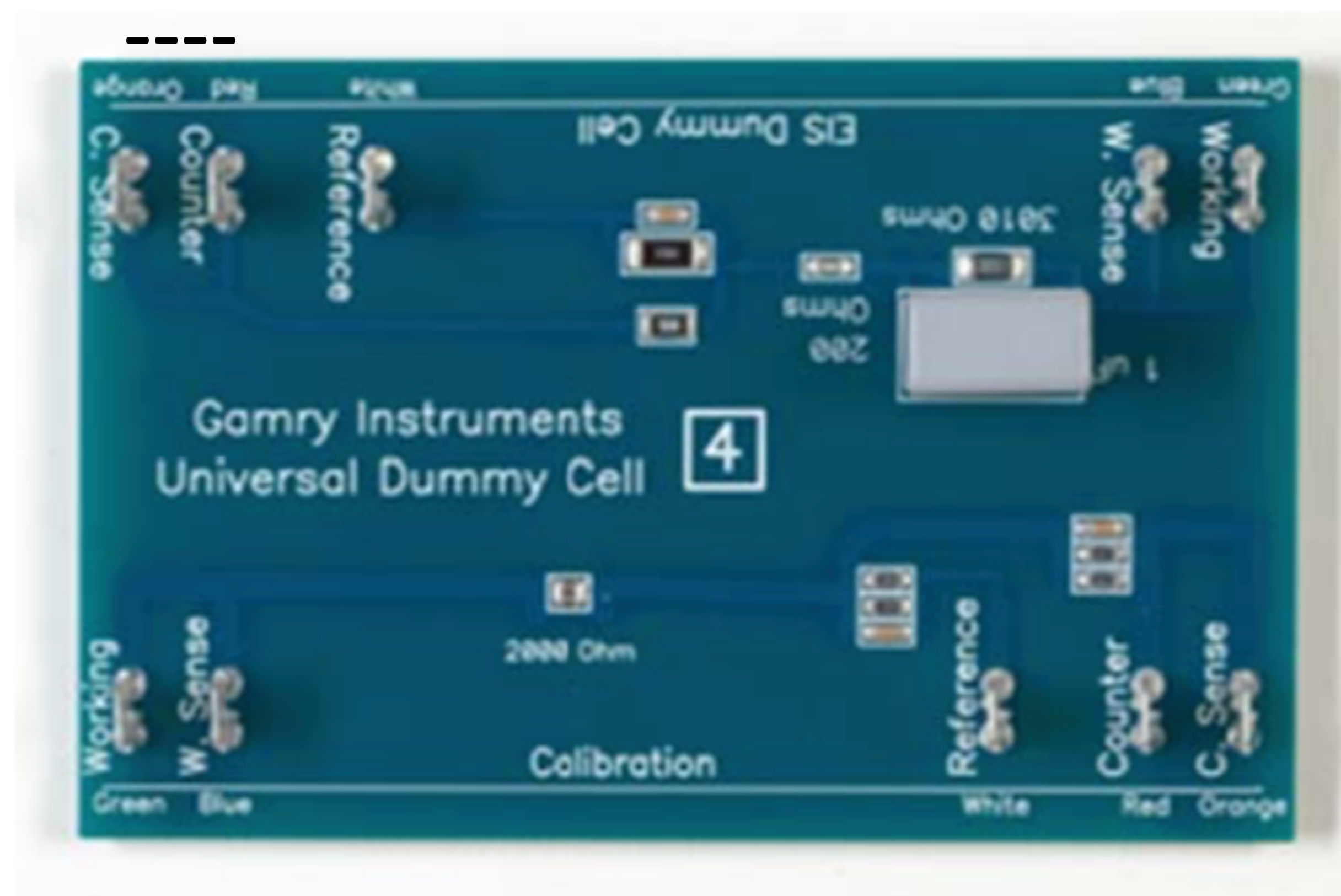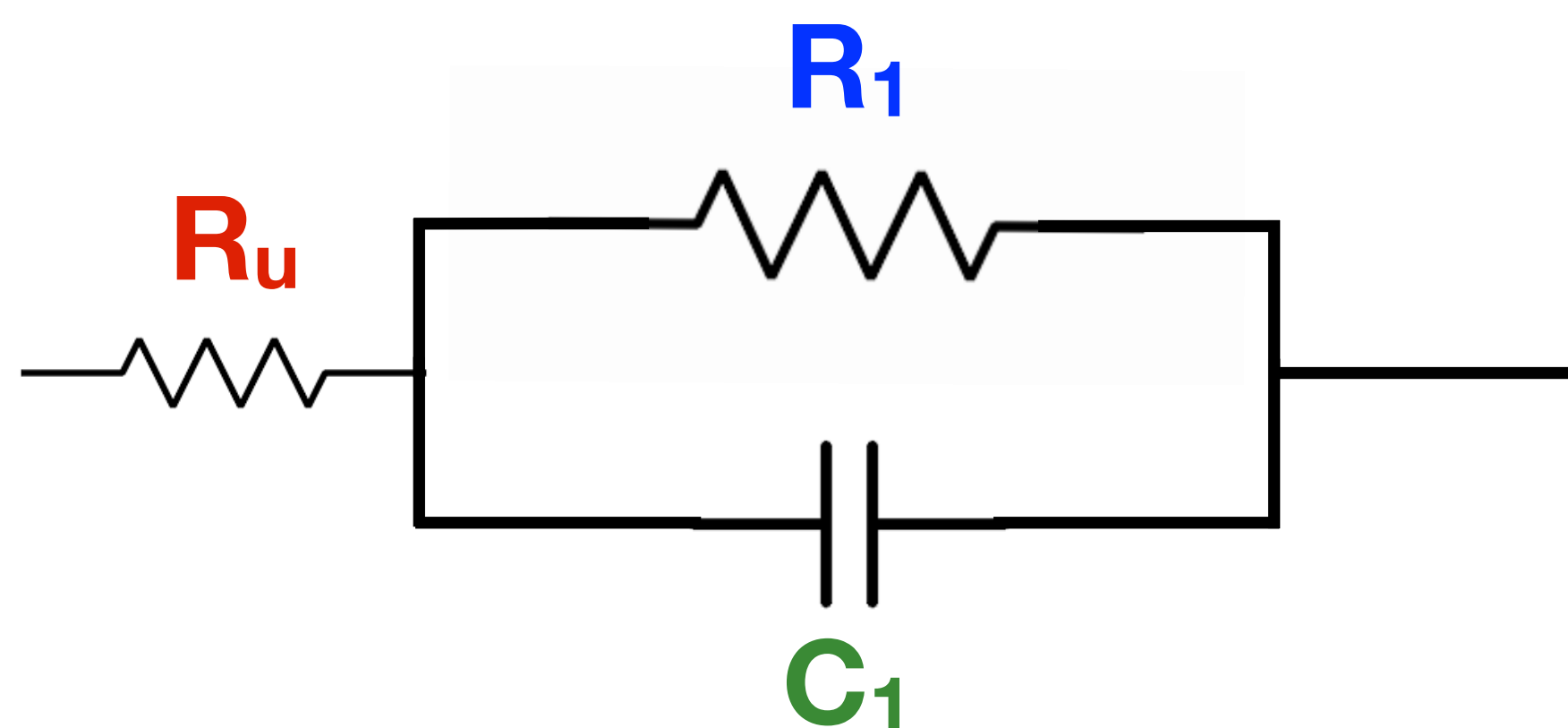R_u 2.95 k Ω — 3.07 k Ω
 R_1 196 Ω — 204 Ω
 C_1 0.9 μ F — 1.10 μ F






Impedance Applications

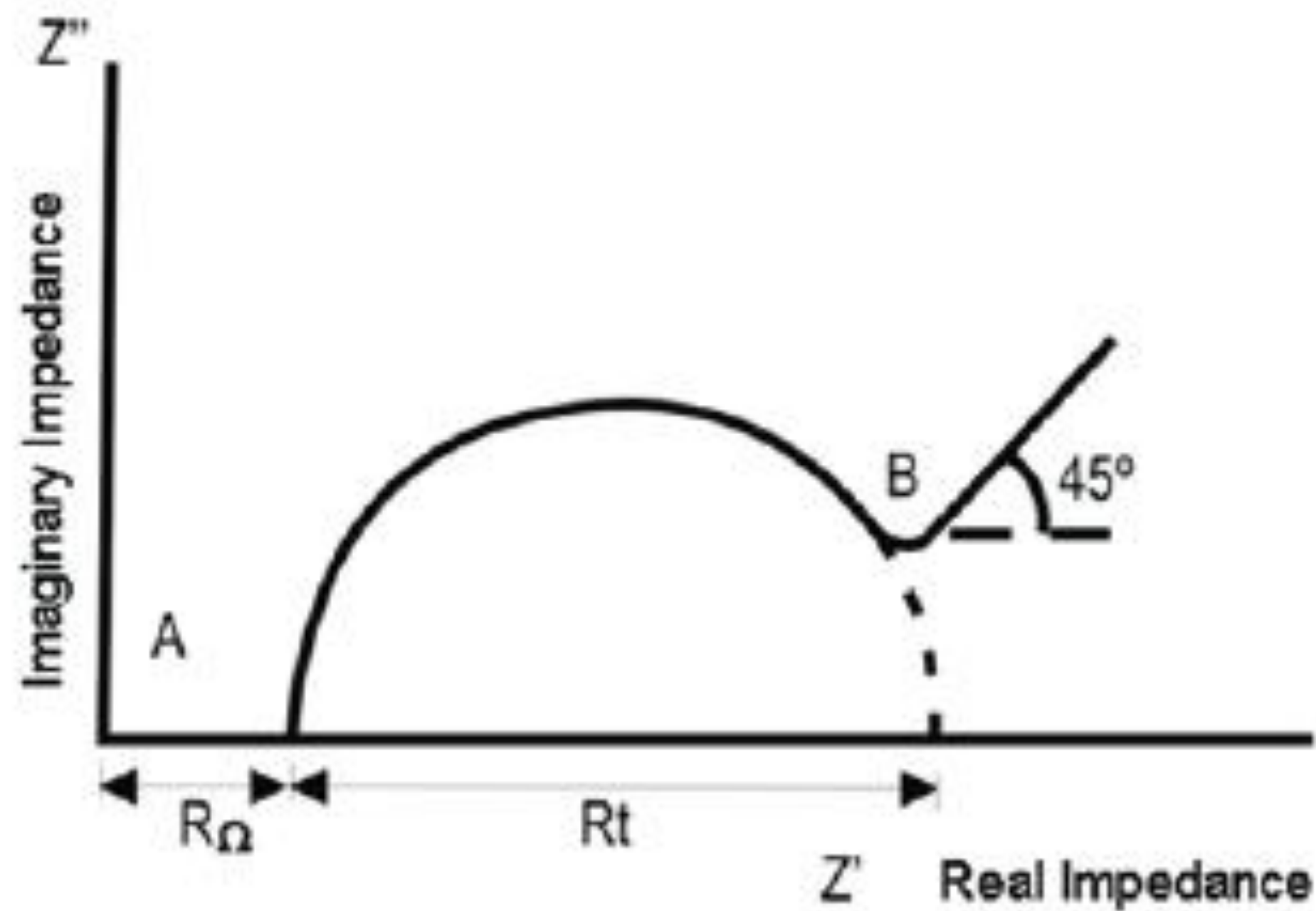

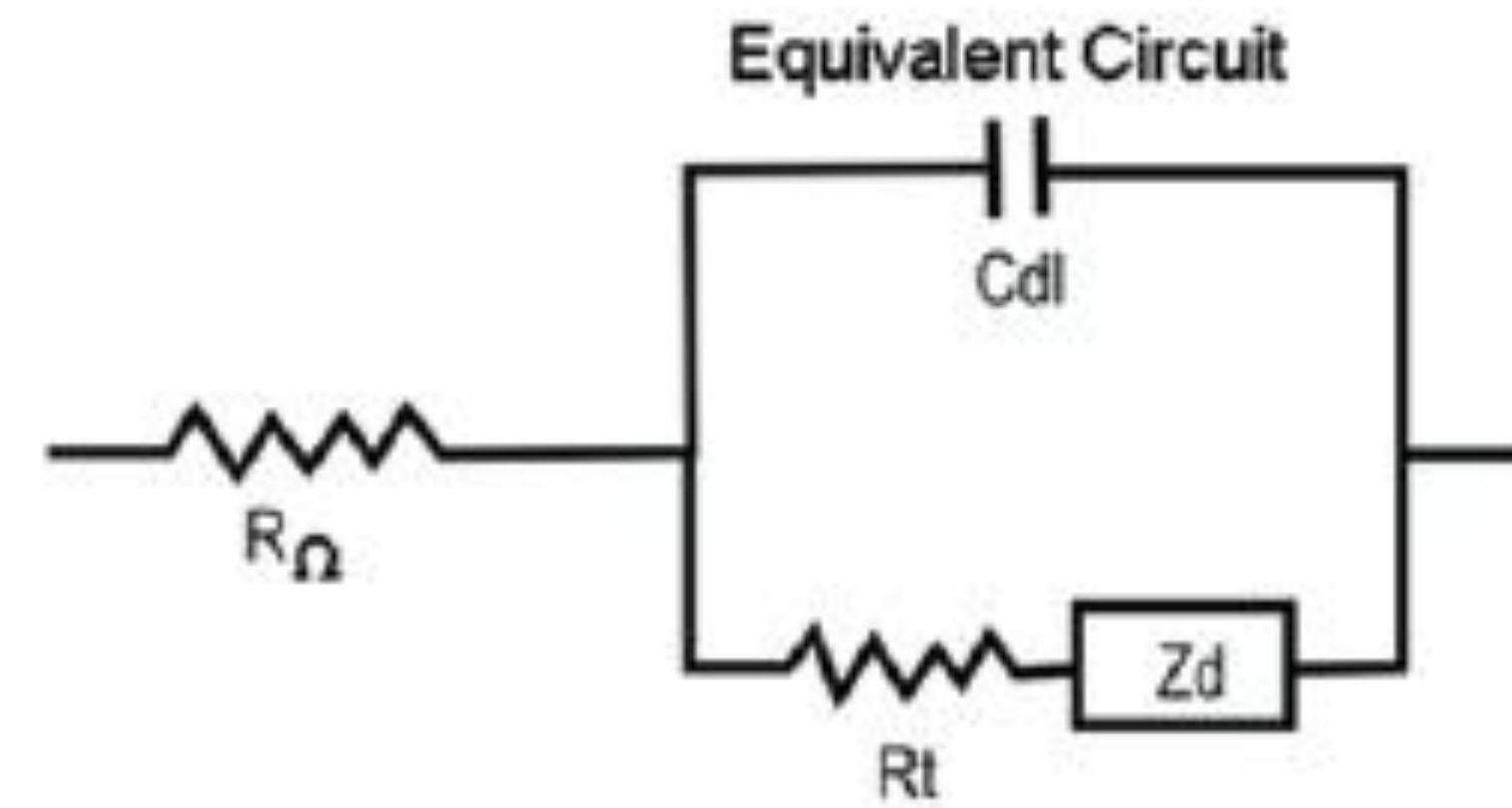A = region of high frequencies (MHz – KHz)
B = region of low frequencies (Hz – μ Hz)





Butler- Volmer Equation

$$i = i_0 \left(\exp\left(\alpha \frac{nF}{RT} \eta\right) - \exp\left(-\left(1-\alpha\right) \frac{nF}{RT} \eta\right) \right)$$

Low Overpotential

$$e^x \rightarrow (1 + x)$$

$$R_{ct} = \frac{RT}{nFi_0}$$

Used to calculate i_0 (*exchange current density*)
Good Representation of catalytic activity of the electrode surface toward a specific redox couple

